

## Series Parallel Circuits

### Equipment

1	Modular Circuits	EM-3536-KIT
1	Modular Current Sensor	EM-3534
1	Voltage Sensor	UI-5100
1	4mm Banana Plug Cords-Red Set of 5	SE-9750
Required but not included:		
1	550 Universal Interface	UI-5001

### Introduction

Series/Parallel circuits are reduced to an equivalent resistance and that resistance is verified by measuring the total current and total voltage.

In a second stand-alone experiment, the behavior of lamps in series, parallel, and series/parallel is qualitatively examined.

### Theory


A resistor generally means a device that obeys Ohm's Law (many devices do not) and has a resistance  $R$ . Two (or more) resistors can be connected in series (as in Figure 1), or in parallel (as in Figure 2). Resistors could also be connected in a series/parallel circuit as shown in Figures 3 and 4. An equivalent resistor is a single resistor that could replace a more complex circuit and produce the same total current when the same total voltage is applied. For a series circuit, the resistances are additive:

$$R_{eq} = R_1 + R_2 \quad (2)$$


where  $R_{eq}$  is the equivalent resistance. For a parallel circuit, the resistances add as reciprocals

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (3)$$

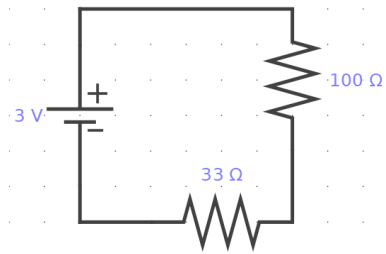
A more complex circuit like that in Circuit Diagram 3 can be handled by noting that  $R_1$  and  $R_2$  are in parallel and can be reduced to an equivalent resistance using Equation 3. That equivalent resistance is then in series with  $R_3$  and can be treated using Equation 2 to find the equivalent resistance of the entire series/parallel circuit.



Circuit Diagram 1: Series

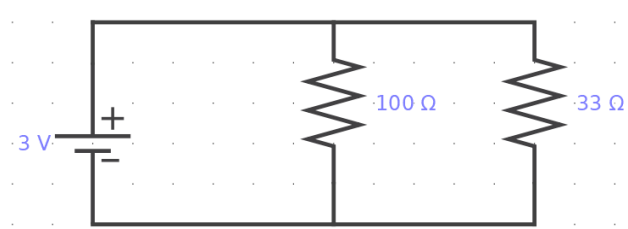


Circuit Diagram 2: Parallel

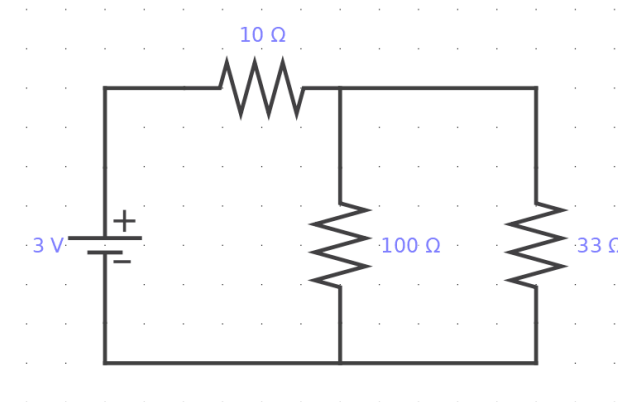

Circuit Diagram 3: Series and Parallel

### Checking the Resistance

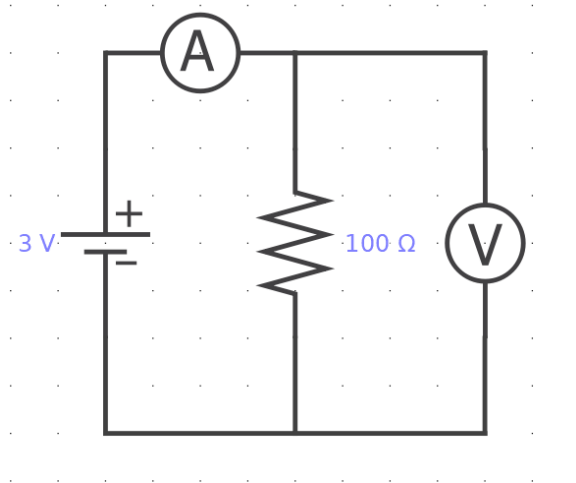1. Plug a Voltage Sensor into Channel A of the 550 Interface.
2. Assemble the circuit for a single resistor as shown in Circuit Diagram 4.



Circuit Diagram 4

3. Turn on the Wireless Current Module and connect it in the software.
4. Set the common sample rate for 500 Hz.


5. Create a graph of Voltage vs. Current.
6. Click open the Signal Generator at the left of the page. Set Waveform for a Triangle wave at 0.1 Hz with an amplitude of 3 V. Click Auto. Click Signal Generator to close the panel.
7. Set a stop condition of 9 seconds.
8. Click Record.
9. On the graph, select a linear fit.
10. The slope of the line is the measured resistance. Record the value of the resistance.
11. Repeat for each of the three resistor modules (100  $\Omega$ , 33  $\Omega$ , and 10  $\Omega$ ).

## Equivalent Resistance

Using the calibrated values for the resistors, calculate the equivalent resistance for each of the three circuit diagrams shown in the Theory Section. Record these equivalent resistances.
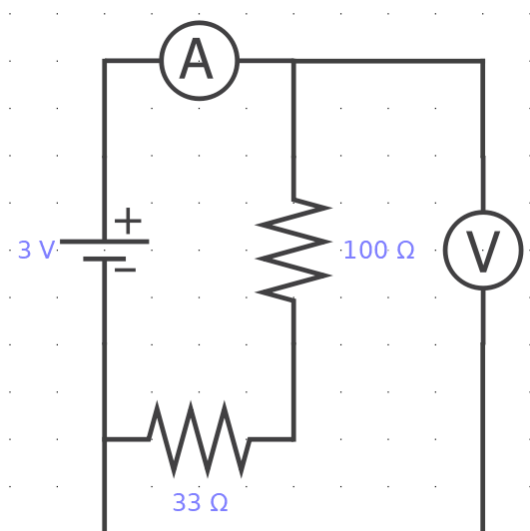
## Setup

Construct the circuit shown in the Circuit Diagram 1 and Figure 1.



Circuit Diagram 1: Series with Meters


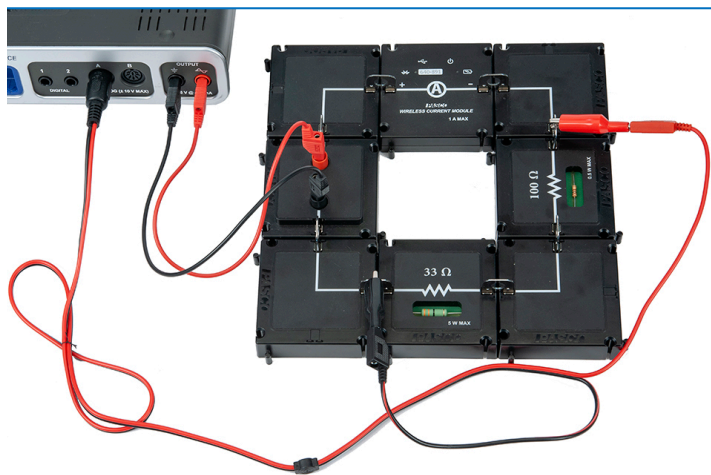


Figure 1: Series Circuit

## Procedure

1. Use the same signal generator settings and Voltage vs. Current graph as before.
2. Start recording for the Series Circuit Diagram.
3. On the graph, select a linear fit.

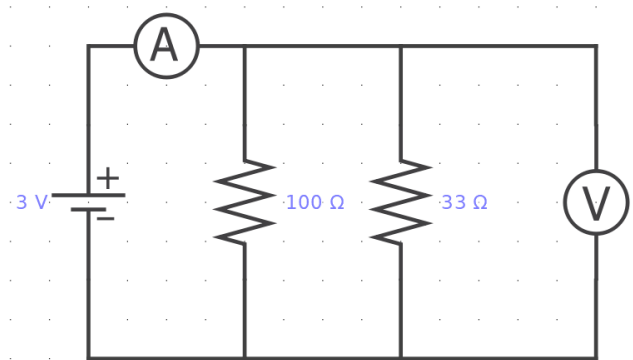4. The slope of the line is the measured equivalent resistance. Record the value of the resistance.
5. Repeat for each of the circuits shown below.



Circuit Diagram 2 with Meters


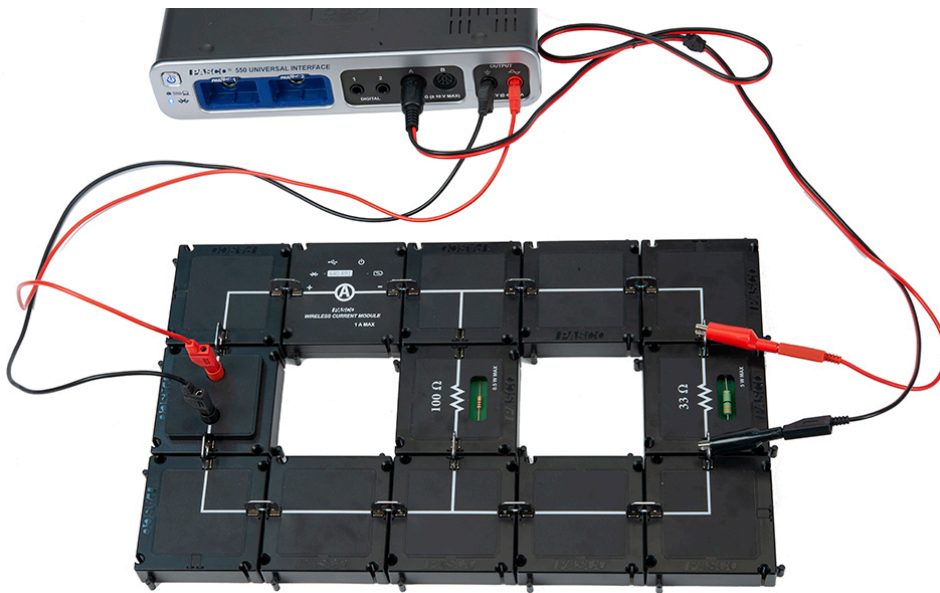


Figure 2: Parallel Resistors with Meters

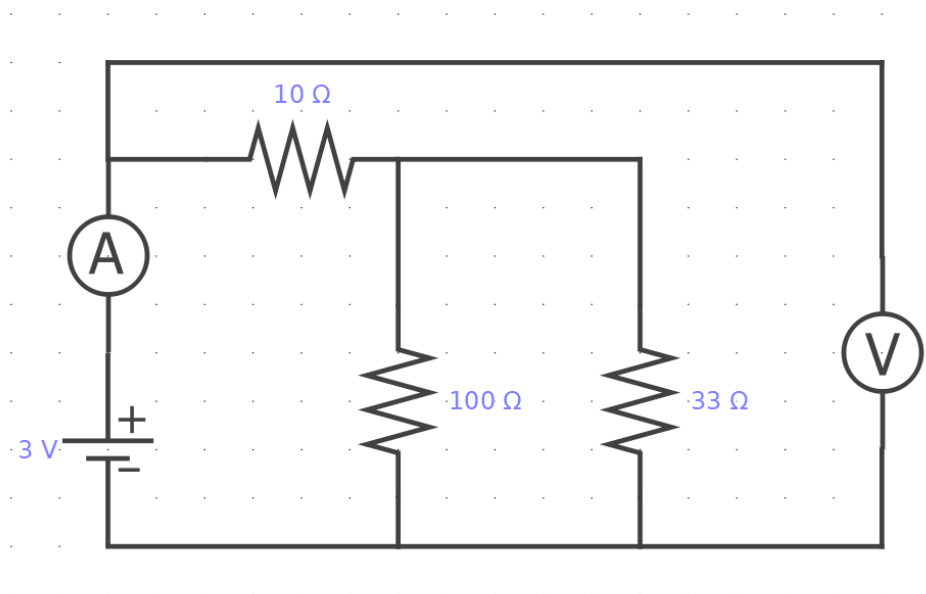


Circuit Diagram 3: Series and Parallel Resistors with Meters

## Conclusions


How well did the experiment work? What does it show?
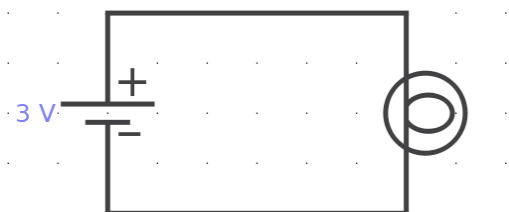
## Lamp Setups


Setup as in Circuit Diagram 5 with only lamp A in the circuit.



Circuit Diagram 5: Single Lamp

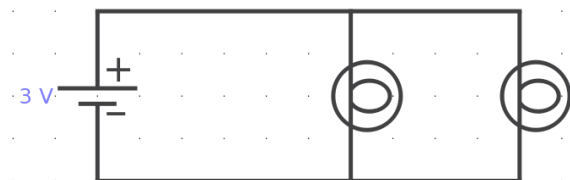

Circuit Diagram 6: Lamps in Parallel

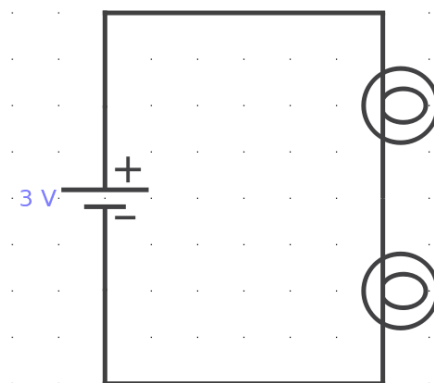

Circuit Diagram 7: Lamps in Series

## Lamp Procedure

1. Turn on the signal generator to 3 VDC. Observe the brightness of the single lamp.
2. Construct Circuit Diagram 6 with two lamps in parallel.
3. Turn on the signal generator to 3 VDC. Observe the brightness of the two lamps. How does the brightness of these lamps compare to the brightness of one bulb? Why?
4. Construct Circuit Diagram 7 with two lamps in series.
5. Turn on the signal generator to 3 VDC. Observe the brightness of the two lamps. How does the brightness of these lamps compare to the brightness of one bulb? Why?